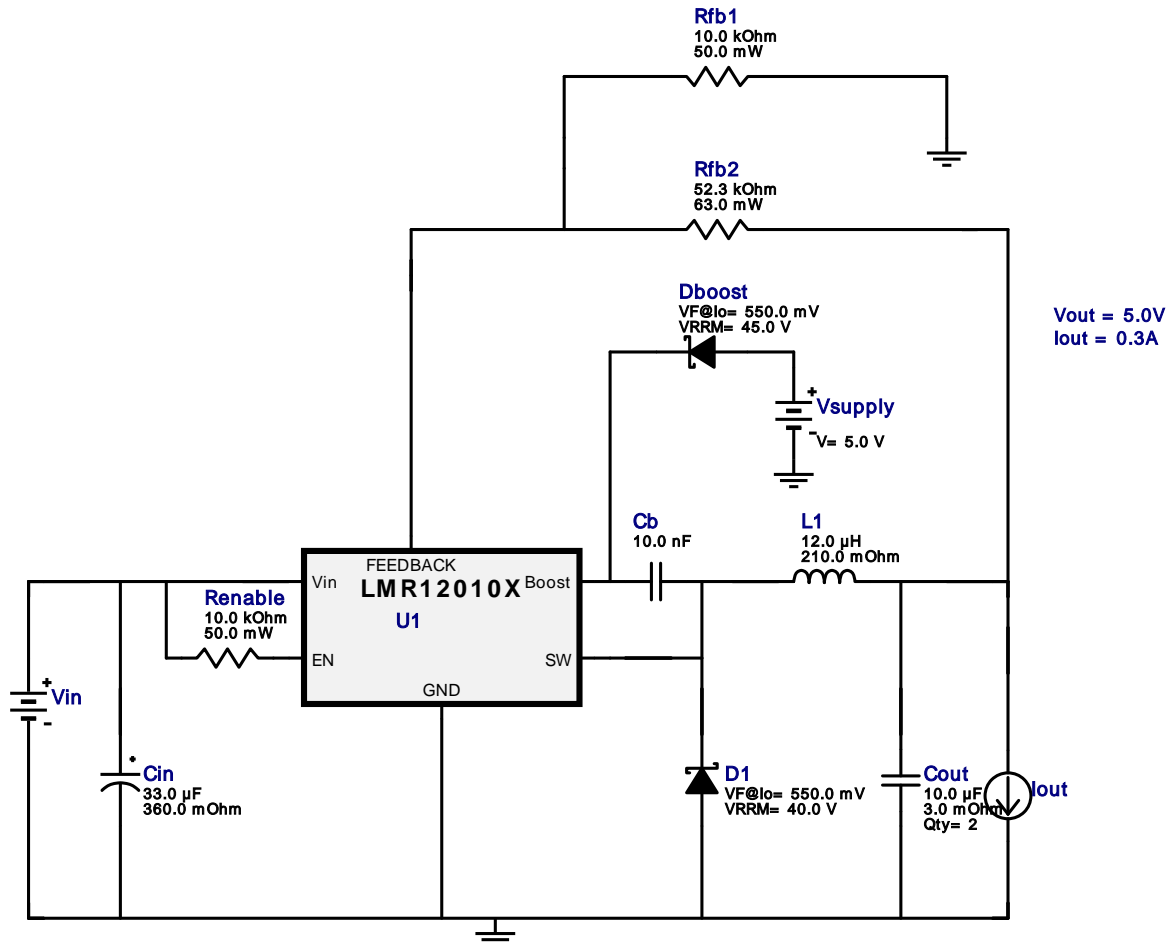


# WEBENCH<sup>®</sup> Design Report

Design : 10 LMR12010XMK/NOPB  
LMR12010XMK/NOPB 12V-12V to 5.00V @ 0.3A

VinMin = 12.0V  
VinMax = 12.0V  
Vout = 5.0V  
Iout = 0.3A






Device = LMR12010XMK/NOPB  
Topology = Buck  
Created = 2022-04-03 06:25:31.662  
BOM Cost = \$1.41  
BOM Count = 11  
Total Pd = 0.2W




1. The Boost pin voltage must be supplied from a source of less than 5.5V. Recommended methods are described in the LM2734 datasheet Application Information.

## Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cb	TDK	CGA4C2C0G1H103J060AA Series= C0G/NP0	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.06	0805 7 mm <sup>2</sup>
Cin	Panasonic	EEE-FK1E330P Series= FK	Cap= 33.0 uF ESR= 360.0 mOhm VDC= 25.0 V IRMS= 240.0 mA	1	\$0.11	SM_RADIAL_D 84 mm <sup>2</sup>
Cout	Kemet	C0805C106K8PACTU Series= X5R	Cap= 10.0 uF ESR= 3.0 mOhm VDC= 10.0 V IRMS= 11.43 A	2	\$0.03	0805 7 mm <sup>2</sup>
D1	Fairchild Semiconductor	SS14FL	VF@Io= 550.0 mV VRRM= 40.0 V	1	\$0.04	SOD-123F 12 mm <sup>2</sup>
Dboost	Bourns	CD0603-B0240	VF@Io= 550.0 mV VRRM= 45.0 V	1	\$0.09	Diode_0603 5 mm <sup>2</sup>

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
L1	NIC Components	NPI43C120MTRF	L= 12.0 $\mu$ H 210.0 mOhm	1	\$0.09	 IND_NPI43C 31 mm <sup>2</sup>
Renable	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm <sup>2</sup>
Rfb1	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm <sup>2</sup>
Rfb2	Vishay-Dale	CRCW040252K3FKED Series= CRCW..e3	Res= 52.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm <sup>2</sup>
U1	Texas Instruments	LMR12010XMK/NOPB	Switcher	1	\$0.93	 MK06A 11 mm <sup>2</sup>


IC Tj

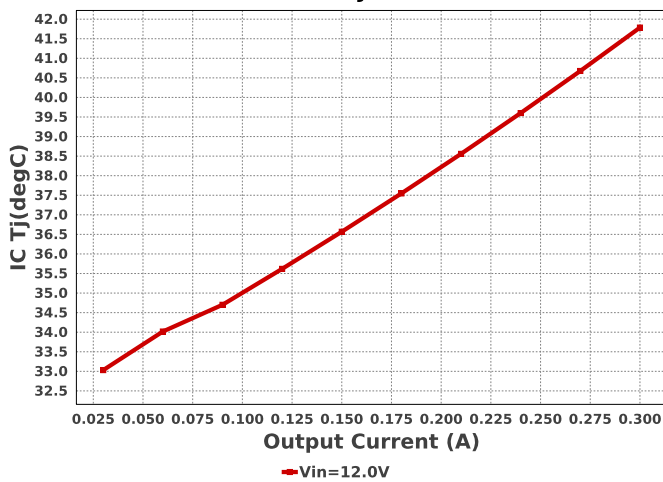


Duty Cycle






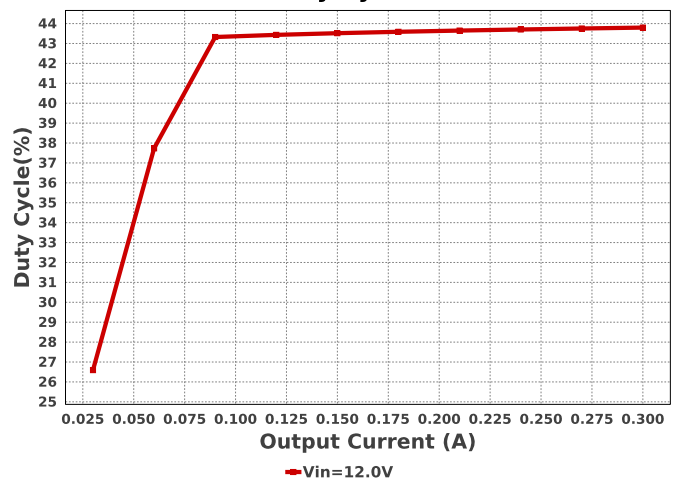








Cin IRMS

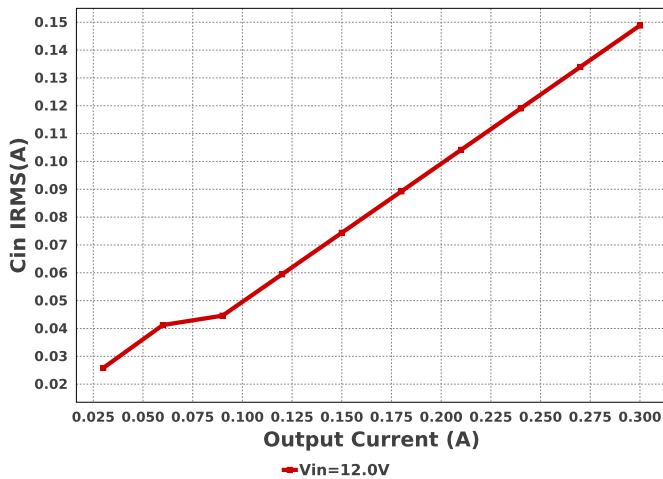


IC Ipk

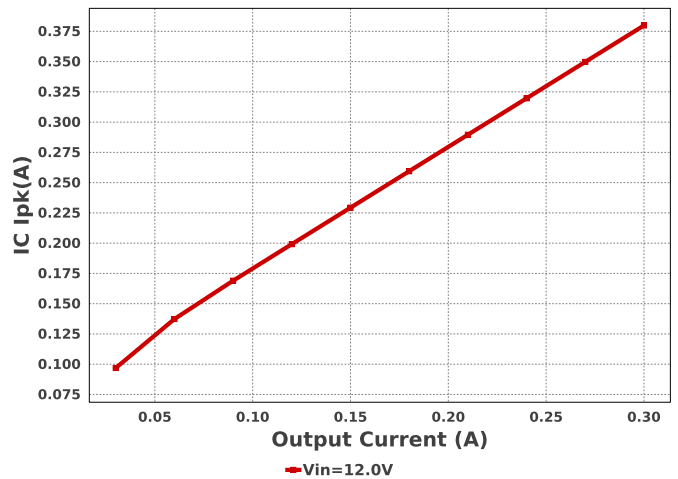

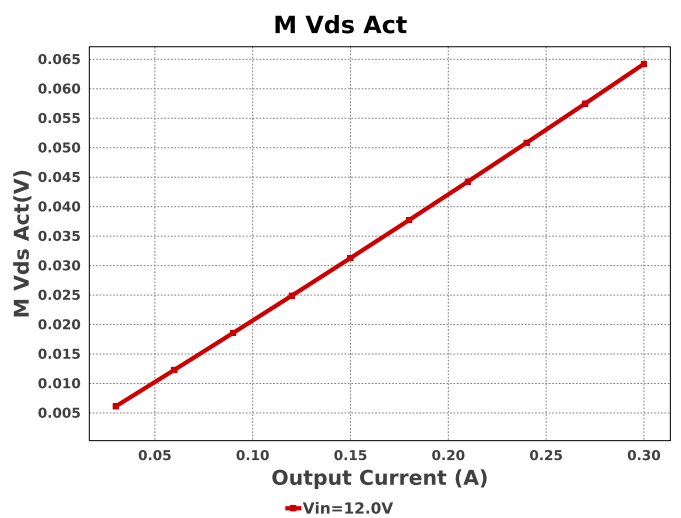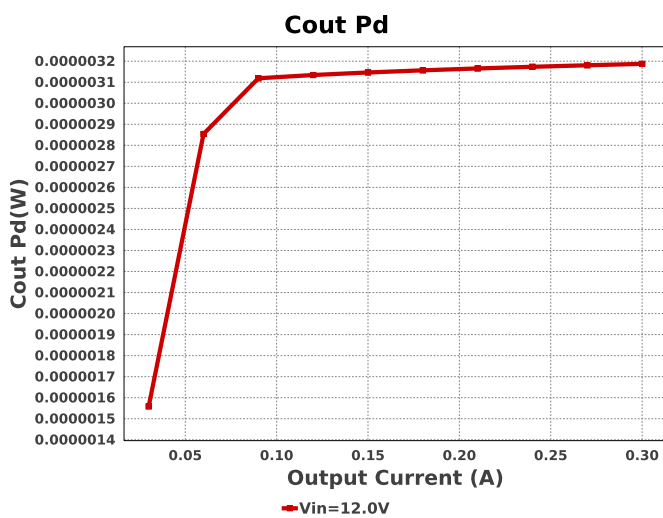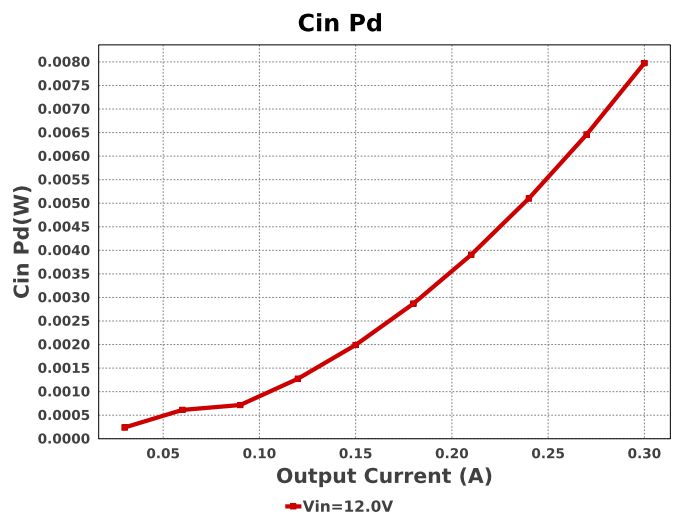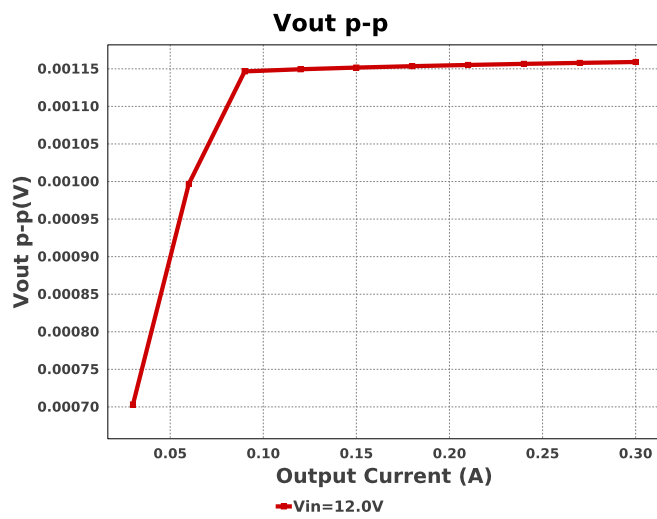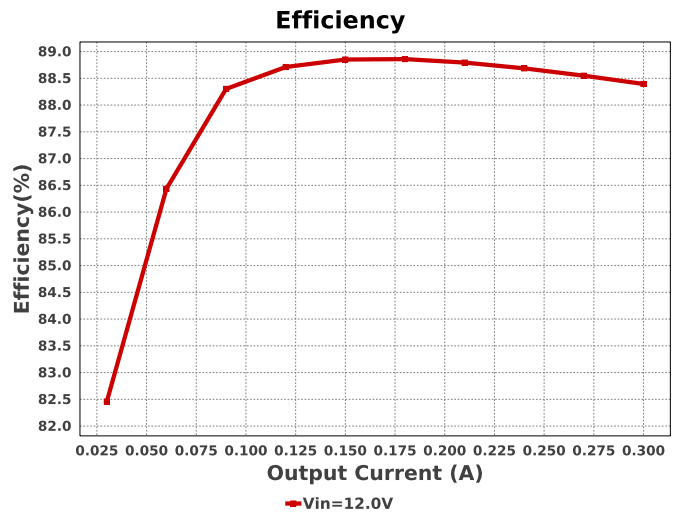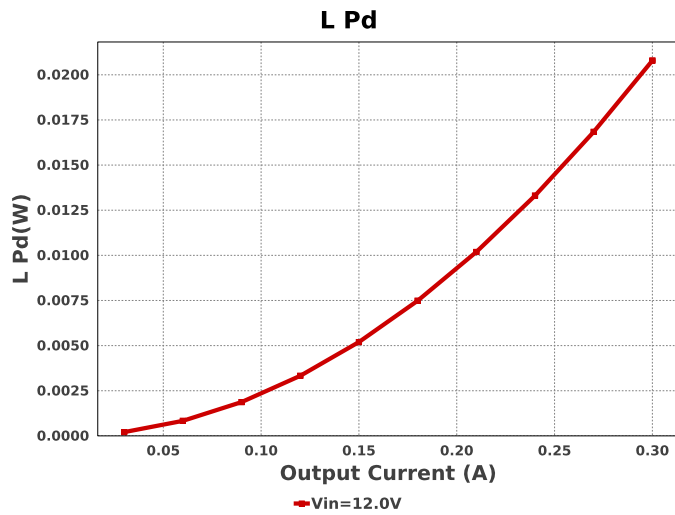

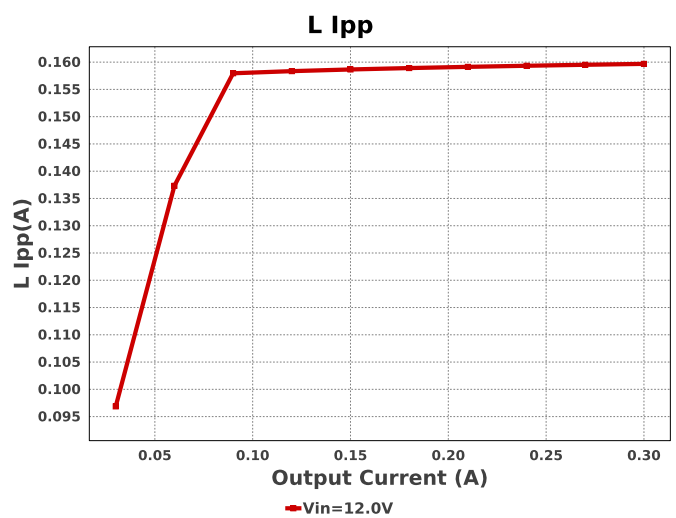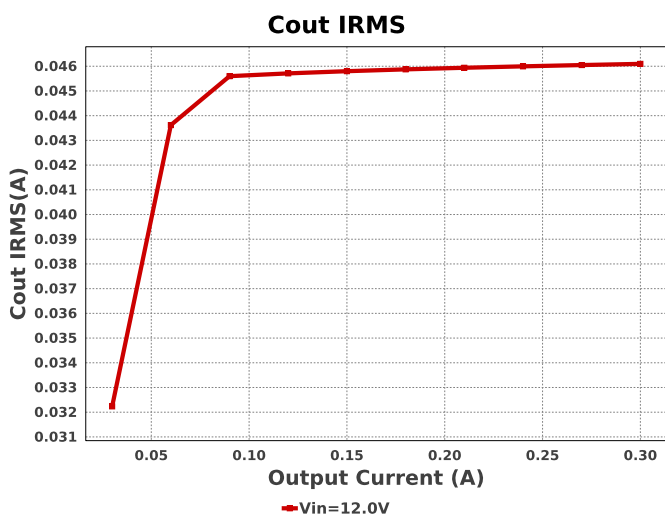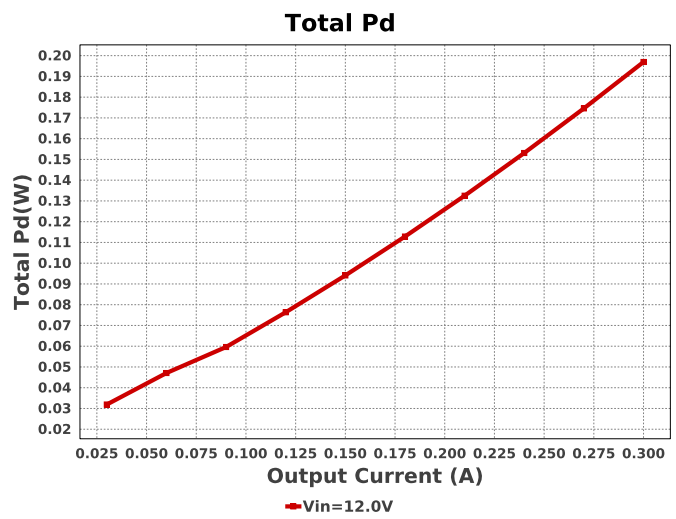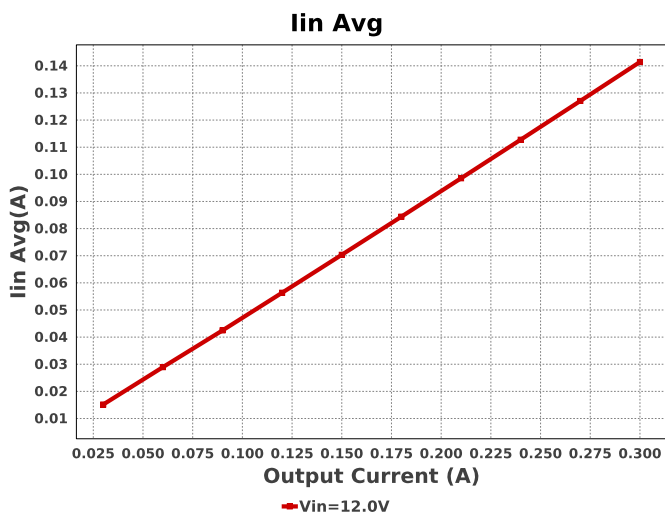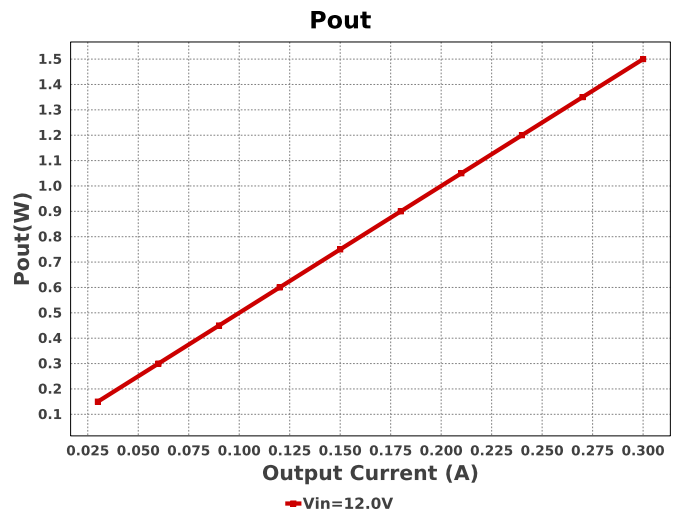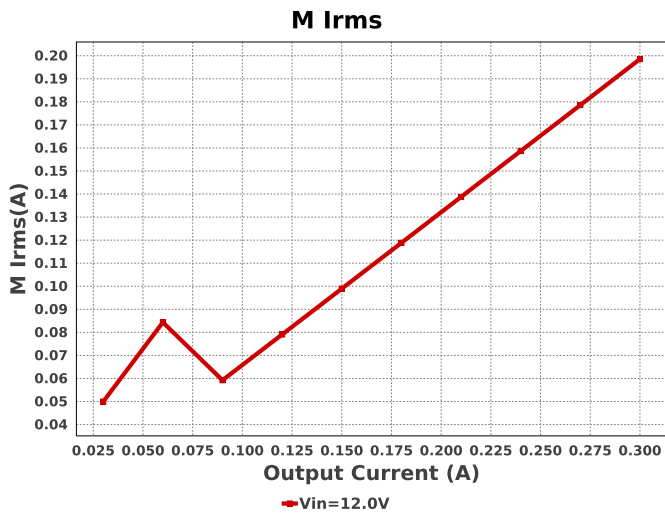

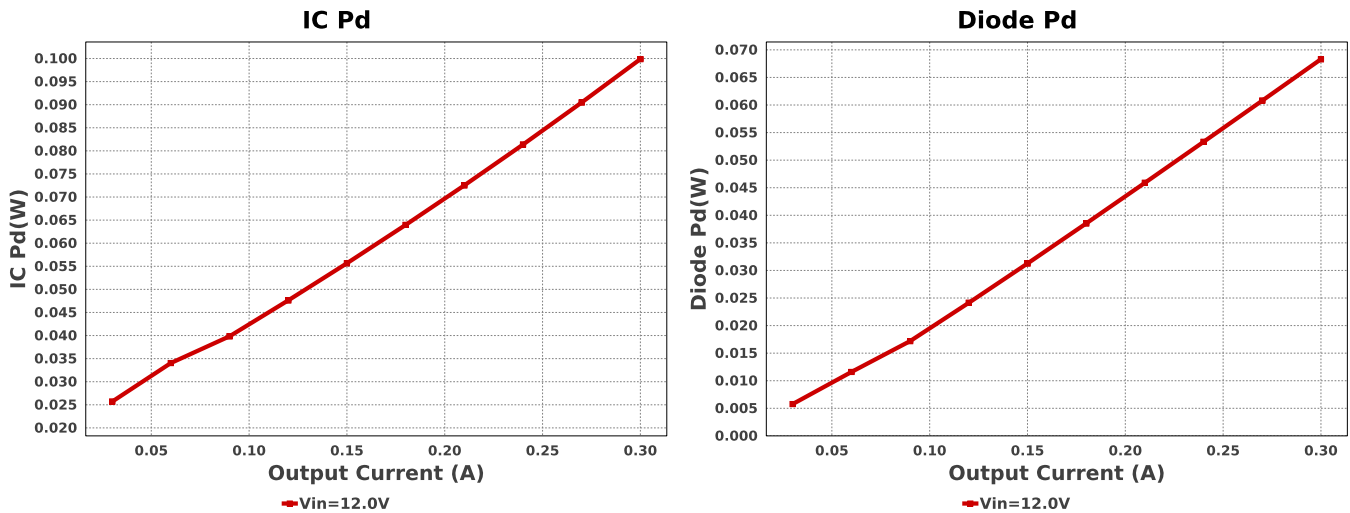

## Operating Values

#	Name	Value	Category	Description
1.	BOM Count	11		Total Design BOM count
2.	Total BOM	\$1.411		Total BOM Cost
3.	Cin IRMS	148.842 mA	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	7.975 mW	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	46.096 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	3.187 $\mu$ W	Capacitor	Output capacitor power dissipation
7.	Diode Pd	68.304 mW	Diode	Diode power dissipation
8.	IC Ipk	379.841 mA	IC	Peak switch current in IC
9.	IC Pd	99.872 mW	IC	IC power dissipation
10.	IC Tj	41.785 degC	IC	IC junction temperature
11.	IC Tolerance	16.0 mV	IC	IC Feedback Tolerance
12.	ICThetaJA	118.0 degC/W	IC	IC junction-to-ambient thermal resistance
13.	Iin Avg	141.41 mA	IC	Average input current
14.	L Ipp	159.682 mA	Inductor	Peak-to-peak inductor ripple current
15.	L Pd	20.79 mW	Inductor	Inductor power dissipation
16.	M Irms	198.541 mA	Mosfet	MOSFET RMS ripple current
17.	M Vds Act	64.228 mV	Mosfet	
18.	Cin Pd	7.975 mW	Power	Input capacitor power dissipation
19.	Cout Pd	3.187 $\mu$ W	Power	Output capacitor power dissipation
20.	Diode Pd	68.304 mW	Power	Diode power dissipation
21.	IC Pd	99.872 mW	Power	IC power dissipation
22.	L Pd	20.79 mW	Power	Inductor power dissipation
23.	Total Pd	196.945 mW	Power	Total Power Dissipation
24.	Duty Cycle	43.798 %	System	Duty cycle
25.	Efficiency	88.394 %	Information	Steady state efficiency
26.	FootPrint	170.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
27.	Frequency	1.6 MHz	Information	Switching frequency
28.	Iout	300.0 mA	System	Iout operating point
29.	Mode	CCM	Information	Conduction Mode
30.	Pout	1.5 W	System	Total output power
31.	Vin	12.0 V	Information	Vin operating point
32.	Vout Actual	4.984 V	System	Vout Actual calculated based on selected voltage divider resistors
33.	Vout Tolerance	3.73 %	Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
34.	Vout p-p	1.159 mV	System	Peak-to-peak output ripple voltage

## Design Inputs

Name	Value	Description
Iout	300.0 m	Maximum Output Current
VinMax	12.0	Maximum input voltage
VinMin	12.0	Minimum input voltage

Name	Value	Description
Vout	5.0	Output Voltage
base_pn	LMR12010X	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

## WEBENCH® Assembly

### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of  $C_{in}$  and  $C_{out}$ , and the inductance and DC resistance of  $L1$  before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

### Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 12.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to  $V_{in}$  and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from  $V_{out}$  and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.
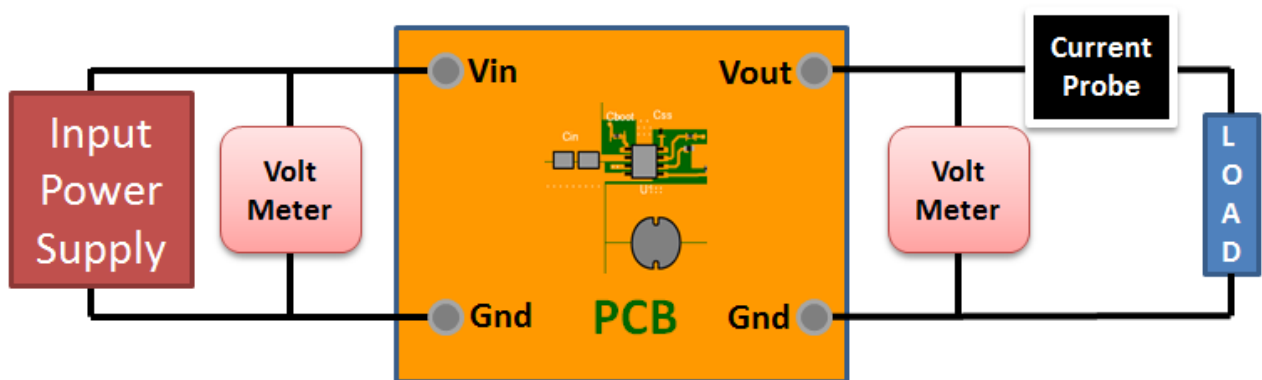
### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between  $V_{in}$  and GND, a load is connected between  $V_{out}$  and GND and a current meter is connected in series between  $V_{out}$  and the load. The load must be able to handle at least rated output power + 50% ( 7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



### Design Assistance

1. Master key : E4B9CFD1C57BC38D[v1]
2. **LMR12010X** Product Folder : <http://www.ti.com/product/LMR12010> : contains the data sheet and other resources.

**Important Notice and Disclaimer**

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.